



**Tribhuvan University**  
**Faculty of Humanities & Social Sciences**  
**OFFICE OF THE DEAN**  
**2019**

**Bachelor in Computer Applications**  
**Course Title: Digital Logic**  
**Code No: CACS 105**  
**Semester: 1<sup>st</sup>**

**Full Marks: 60**  
**Pass Marks: 24**  
**Time: 3 hours**

**Centre:**

**Symbol No:**

**Candidates are required to answer the questions in their own words as far as possible.**

**Group A**

**Attempt all the questions.**

**[10×1 = 10]**

1. Circle (O) the correct answer.

- i) Which one of the following is hexadecimal equivalent of  $(5073.052)_8$ ?
  - a) A3C.150
  - b) B2B.140
  - c) A3B.150
  - d) B3A.150
- ii) Which one of the following is 9's complement of  $(3578.501)_{10}$ ?
  - a) 4926.947
  - b) 3926.947
  - c) 4926.937
  - d) None of the Above
- iii) Which one of the following is the equivalent reflected code of 1101?
  - a) 1001
  - b) 1011
  - c) 1000
  - d) 1010
- iv) When output will go high in NOR Gate?
  - a) if all inputs are high
  - b) if any input is high
  - c) if any input is low
  - d) if all inputs are low
- v) According to Boolean algebra: What is the value of  $X + 1 = ?$ 
  - a)  $\bar{X}$
  - b) 1
  - c) 0
  - d)  $X$
- vi) The logic circuits whose outputs at any instant of time depends only on the present input but also on the past outputs are called
  - a) Combinational circuits
  - b) Sequential circuits
  - c) Latches
  - d) Flip-flops

- vii) If  $Q = 1$ , the output is said to be
- a) Reset
  - b) Set
  - c) Previous state
  - d) current state
- viii) Which one of the following are also called ripple counters?
- a) SSI counters
  - b) Synchronous counters
  - c) Asynchronous counters
  - d) VLSI counters
- ix) How many flip-flops are required to construct MOD-30 counter?
- a) 5
  - b) 6
  - c) 4
  - d) 8
- x) How much storage capacity does each stage in a shift register represent?
- a) One bit
  - b) Two bits
  - c) Four bits
  - d) Eight bits



**Tribhuvan University**  
**Faculty of Humanities & Social Sciences**  
**OFFICE OF THE DEAN**  
**2019**

**Bachelor in Computer Applications**  
**Course Title: Digital Logic**  
**Code No: CACS 105**  
**Semester: 1<sup>st</sup>**

**Full Marks: 60**  
**Pass Marks: 24**  
**Time: 3 hours**

**Candidates are required to answer the questions in their own words as far as possible.**

**Group B**

**Attempt any SIX questions.**

**[6×5 = 30]**

2. Subtract:  $1010.110 - 101.101$  using both 2's and 1's complement. [5]
3. Simplify (Using k-map) the given Boolean function in both SOP and POS using the don't care condition d:

$$F(A, B, C, D) = \pi(0,1,3,7,8,12) \text{ and } \pi d(5,10,13,14) \quad [2 + 3]$$

4. Define decoder. Draw logic diagram and truth table of 3 to 8-line decoder. [1 + 4]
5. Define ROM. Implement the following combinational logic function using ROM: [2 + 3]

A1	A0	F1	F2
0	0	1	0
0	1	0	1
1	0	1	1
1	1	1	0

6. What are the drawbacks of clocked RS flip flop? Explain the operation of JK Flip flop along with its circuit diagram and characteristic table. [2+3]
7. What is T flip-flop? Explain clocked JK flip-flop with its logic diagram and truth table. [1 + 4]

8. Design MOD - 7 counter with state and timing diagram. [2 + 1 + 2]

**Group C**

**Attempt any TWO questions.** [2×10 = 20]

9. Define PLA. Design a PLA circuit with given functions.

$$F1 (A, B, C) = \Sigma (3, 5, 6, 7)$$

$$F2 (A, B, C) = \Sigma (0, 2, 4, 7). \text{ Design PLA program table also.} [3 + 7]$$

10. Distinguish between sequential and combinational logic with example? Discuss the design procedure of combinational logic. [4+6]

11. A sequential circuit with two D flip-flops, A and B, two inputs x and y, and one output z, is specified by the following next state and output equations [4+3+3]

$$A(t+1) = x'y + x A$$

$$B(t +1) = x'B + x A$$

$$z = B$$

- Draw the logic diagram.
- Derive the state table.
- Derive the state diagram.